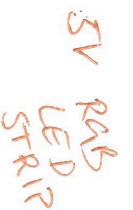



or



LED Screen Match
→ V1.0 Schematic

Note: If your LED strip runs on a high voltage you should use a transistor instead, one for each channel.

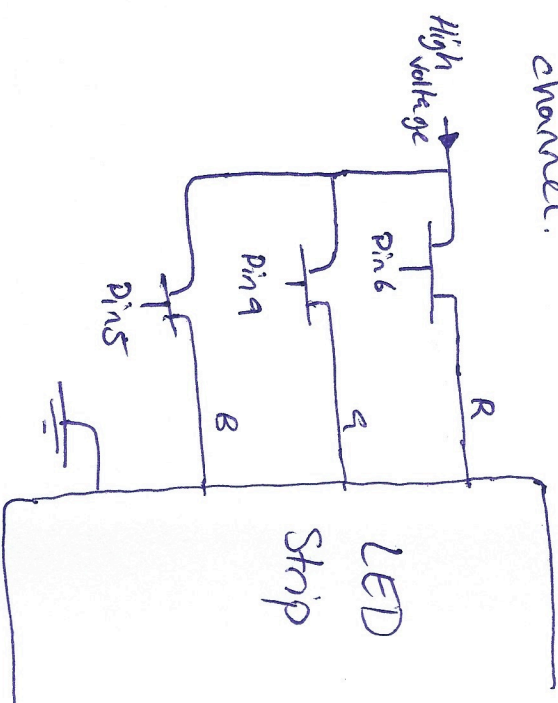Default Pins are for Arduino Mini.
Red → Pin 6
Green → Pin 9
Blue → Pin 5
As long as they are PWM pins + declared in Arduino.ino it will work fine.



Make sure the ground of the LED strip is connected to the ground of the Arduino.